

Computer Architecture Experiment

Topic 8. Cache Design

浙江大学计算机学院
陈文智

chenwz@zju.edu.cn



实验操作流程

- 阅读实验文档，了解Cache的理论内容
- 设计Cache Management Unit和Cache Line。
- 对Cache单元设计测试激励进行仿真，检验Cache单元的仿真结果是否符合要求。



实验验收标准

- 仿真执行过程中，处理器的行为和内部控制信号均符合要求。
- 下载至开发板后的单步执行过程中，寄存器的变化过程和最终执行结果与测试程序相吻合。



Outline

- **Experiment Purpose**
- **Experiment Task**
- **Basic Principle**
- **Operating Procedures**
- **Precaution**
- **Checkpoints**



Experiment Purpose

- Understand **Cache Line**.
- Understand the principle of **Cache Management Unit (CMU)** and **State Machine of CMU**.
- Master the design methods of CMU.
- Master **the design methods** of **Cache Line**.
- master **verification** methods of Cache Line.



Experiment Task

- Design of **Cache Line** and **CMU**.
- **Verify** the Cache Line and CMU.
- **Observe the Waveform** of Simulation.



Cache Line

V	D	tag	Data

Cache Mode

- Direct Map
- Write Back
- Write Allocate





Address

- Bytes of word = 4, WORD_BYTES_WIDTH = 2
- Words of line = 4, LINE_WORDS_WIDTH = 2
- Tag bits = 22
- Address bits = 32
- $\text{LINE_INDEX_WIDTH} = \text{ADDR_BITS} - \text{TAG_BITS} - \text{LINE_WORDS_WIDTH} - \text{WORD_BYTES_WIDTH} = ?$
- Line Number = ?



Cache Line Memory

- `reg [LINE_NUM-1:0] inner_valid = 0;`
- `reg [LINE_NUM-1:0] inner_dirty = 0;`
- `reg [TAG_BITS-1:0] inner_tag [0:LINE_NUM-1];`
- `reg [WORD_BITS-1:0] inner_data [0:LINE_NUM*LINE_WORDS-1];`



Input and output Signals of Cache Line

```
module cache (  
    input wire clk, // clock  
    input wire rst, // reset  
    input wire [ADDR_BITS-1:0] addr, // address  
    input wire store, // set valid to 1 and reset dirty to 0  
    input wire edit, // set dirty to 1  
    input wire invalid, // reset valid to 0  
    input wire [WORD_BITS-1:0] din, // data write in  
    output wire hit, // hit or not  
    output reg [WORD_BITS-1:0] dout, // data read out  
    output reg valid, // valid bit  
    output reg dirty, // dirty bit  
    output reg [TAG_BITS-1:0] tag // tag bits  
);
```



Read and Write Cache

```
dout <= inner_data[addr[ADDR_BITS-TAG_BITS-1:WORD_BYTES_WIDTH]];
```

```
if ( ??? || ???)
```

```
inner_data[addr[ADDR_BITS-TAG_BITS-1:WORD_BYTES_WIDTH]] <= din;
```



Dirty, Valid, tag of Cache

- **invalid**

$\text{inner_valid}[\text{addr}[\text{ADDR_BITS-TAG_BITS-1:LINE_WORDS_WIDTH+WORD_BYTES_WIDTH}]] \leq ?$

$\text{inner_dirty}[\text{addr}[\text{ADDR_BITS-TAG_BITS-1:LINE_WORDS_WIDTH+WORD_BYTES_WIDTH}]] \leq ?$

- **store**

$\text{inner_valid}[\text{addr}[\text{ADDR_BITS-TAG_BITS-1:LINE_WORDS_WIDTH+WORD_BYTES_WIDTH}]] \leq ?$

$\text{inner_dirty}[\text{addr}[\text{ADDR_BITS-TAG_BITS-1:LINE_WORDS_WIDTH+WORD_BYTES_WIDTH}]] \leq ?$

$\text{inner_tag}[\text{addr}[\text{ADDR_BITS-TAG_BITS-1:LINE_WORDS_WIDTH+WORD_BYTES_WIDTH}]] \leq ?$

- **edit**

$\text{inner_dirty}[\text{addr}[\text{ADDR_BITS-TAG_BITS-1:LINE_WORDS_WIDTH+WORD_BYTES_WIDTH}]] \leq ?$

$\text{inner_tag}[\text{addr}[\text{ADDR_BITS-TAG_BITS-1:LINE_WORDS_WIDTH+WORD_BYTES_WIDTH}]] \leq ?$



output of Dirty, Valid, tag, hit

`valid <= inner_valid[addr[ADDR_BITS-TAG_BITS-1:LINE_WORDS_WIDTH+WORD_BYTES_WIDTH]]`

`dirty <= inner_dirty[addr[ADDR_BITS-TAG_BITS-1:LINE_WORDS_WIDTH+WORD_BYTES_WIDTH]]`

`tag <= inner_tag[addr[ADDR_BITS-TAG_BITS-1:LINE_WORDS_WIDTH+WORD_BYTES_WIDTH]]`

`hit = ?? & ??`



Simulation Example

clk=1;

#210 store = 1; din = 32'h11111111; addr = 32'h00000000;

#20 addr = 32'h00000004;

#20 addr = 32'h000000A8;

#20 addr = 32'h0000001C;


#20 store = 0; addr = 32'h000000B4; din = 0;

#100 edit = 1; din = 32'h22222222; addr = 32'h00000008;


#100 edit = 0; din = 0; addr = 0;

initial forever #10 clk = ~clk;

Simulation Example

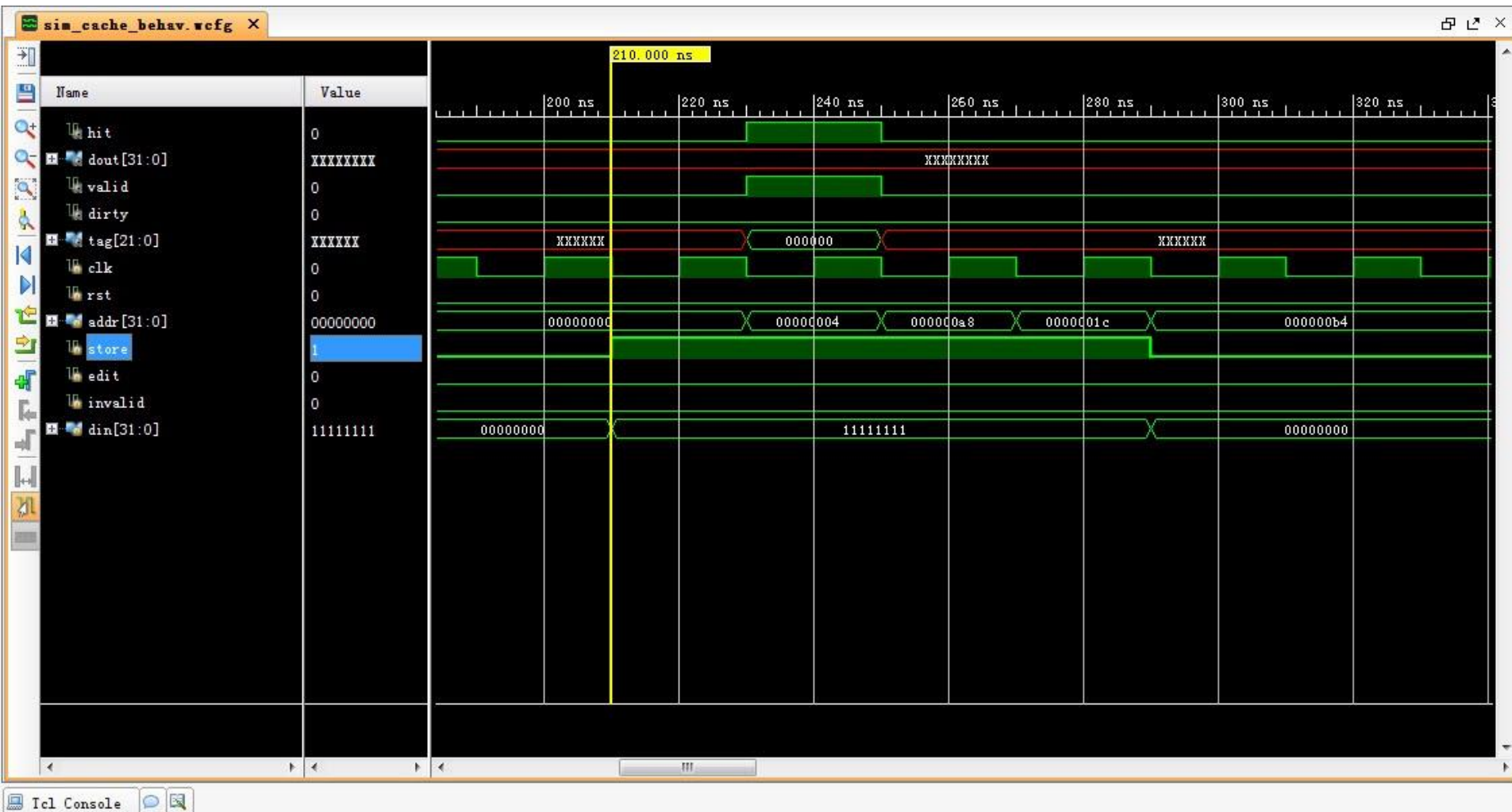

Simulation Example

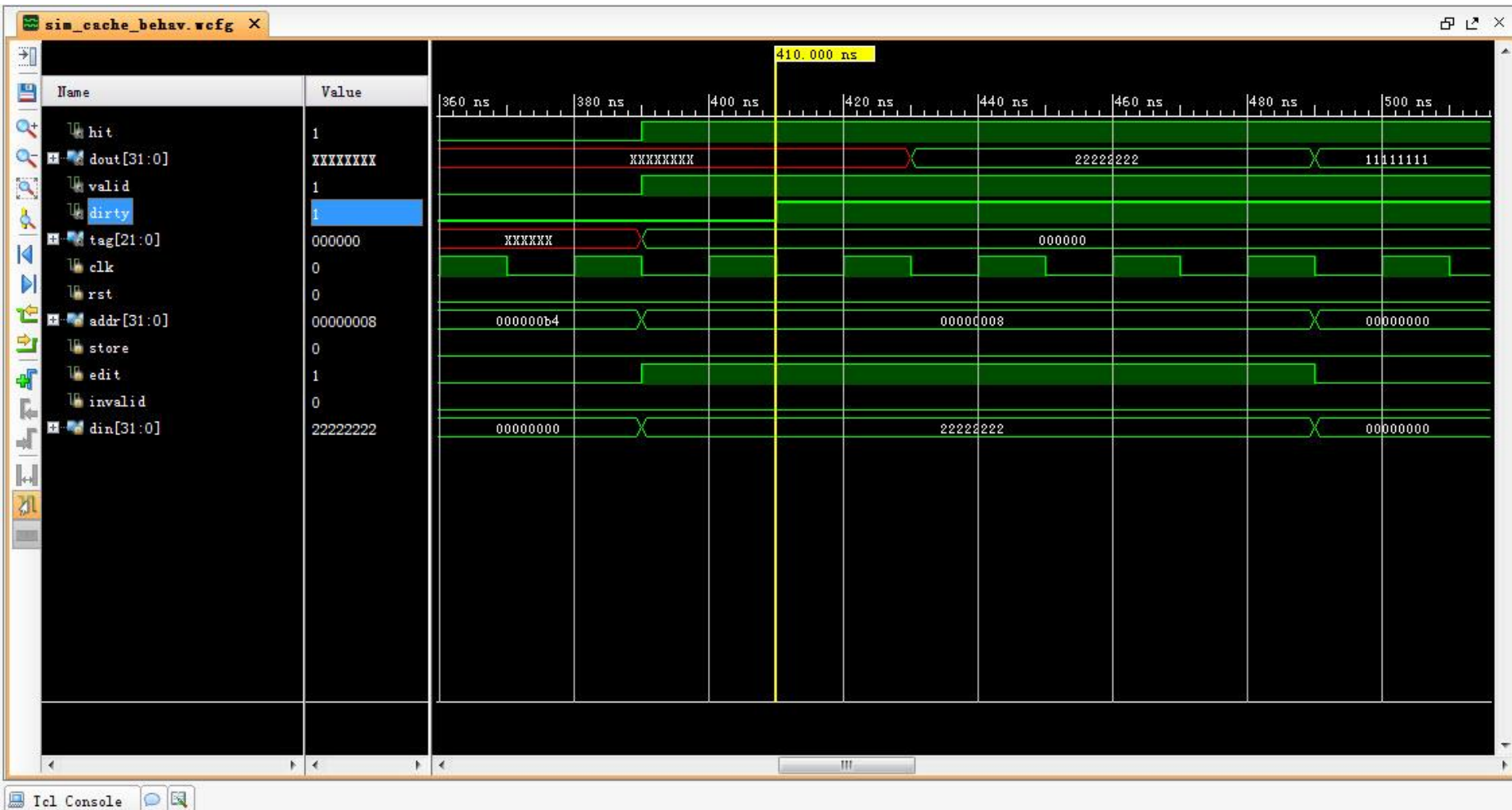

Simulation



- **Write Simulation Code yourself**

- cache initialization

- read

- miss

- hit

- write

- miss

- hit

Cache Management Unit

CPU
Interface

Addr_RW

EN_R

EN_W

Data_W

Data_R

Busy

CMU

Memory
Interface

Mem CS

Mem WE

Mem Addr


Mem_data_o

Mem_data_i


Mem_ack_i

Cache Operati

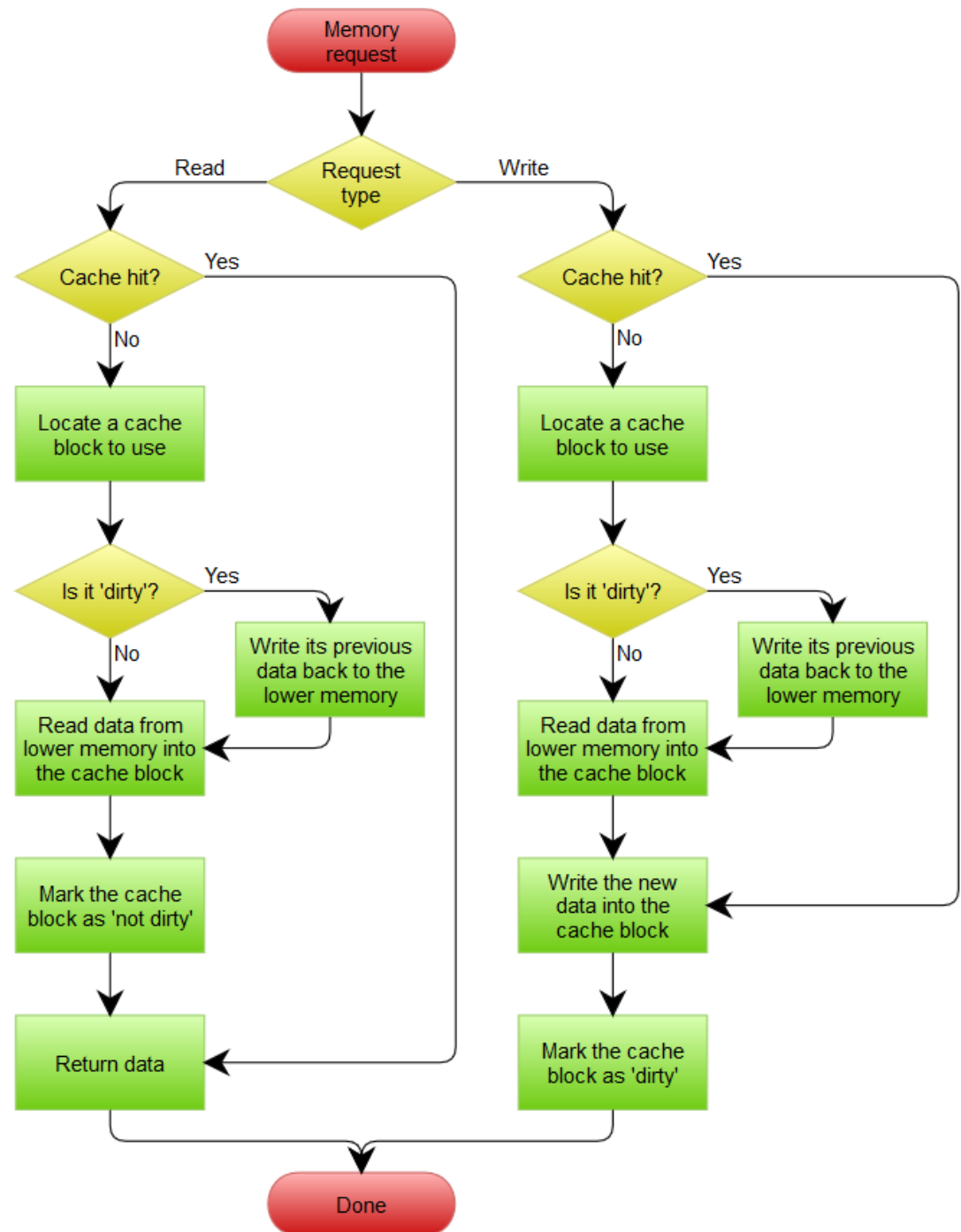- Read (Hit/Miss)
- Write (Hit/Miss)
- Replace (Clean/Dirty)




Cache Management State Machine

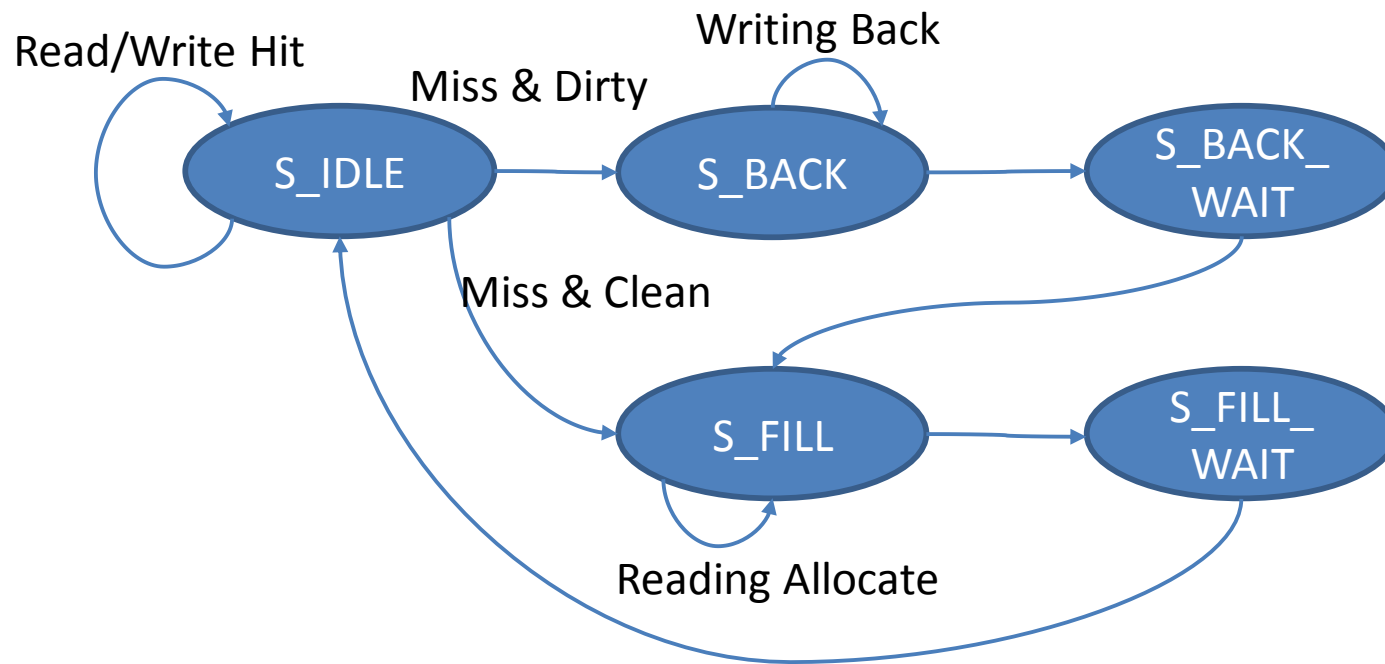

State Machine



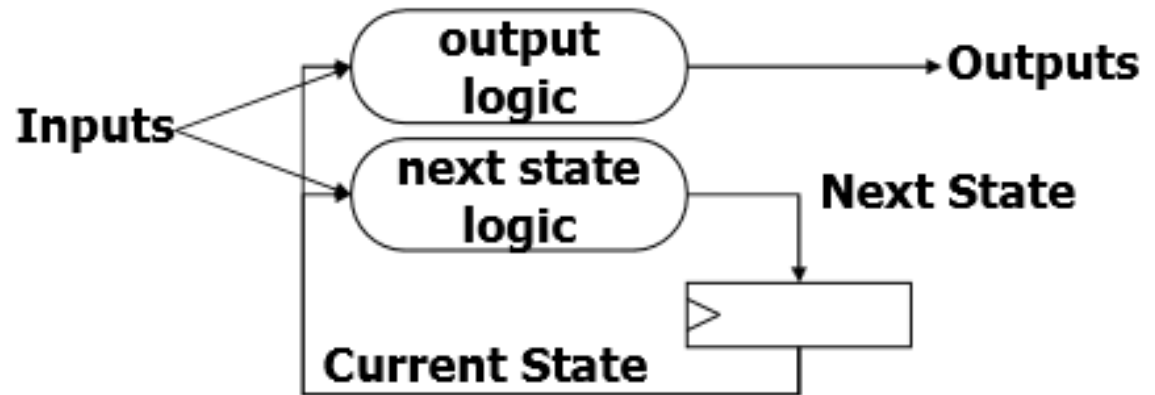- Next State Logic
- State assignment
- Output





Next logic (1)

```
S_IDLE: begin
    if (en_r || en_w) begin
        if (cache_hit)
            next_state = ???;
        else if (cache_valid && cache_dirty)
            next_state = ???;
        else
            next_state = ???;
    end
end
S_BACK: begin
    if (mem_ack_i)
        next_word_count = word_count + 1'h1;
    else
        next_word_count = word_count;
    if (mem_ack_i && word_count == {LINE_WORDS_WIDTH{1'b1}})
        next_state = ???;
    else
        next_state = ???;
```



Next logic (2)

```
S_BACK_WAIT: begin
    next_word_count = 0;
    next_state = ???;
end
S_FILL: begin
    if (mem_ack_i)
        next_word_count = word_count + 1'h1;
    else
        next_word_count = word_count;
    if (mem_ack_i && word_count == {LINE_WORDS_WIDTH{1'b1}})
        next_state = ???;
    else
        next_state = ???;
    end
end
S_FILL_WAIT: begin
    next_word_count <= 0;
    next_state <= ???;
```




Perform State Assignment

```
always @(posedge clk) begin
    if (rst) begin
        state <= 0;
        word_count <= 0;
    end
    else begin
        state <= next_state;
        word_count <= next_word_count;
    end
end
```

Output (1)



```
case (next_state)
    S_IDLE: begin
        cache_addr = addr_rw;
        cache_edit = en_w;
        cache_din = data_w;

    end

    S_BACK, S_BACK_WAIT: begin
        cache_addr = {addr_rw[31:LINE_WORDS_WIDTH+2], next_word_count,
2'b00};

    end

    S_FILL, S_FILL_WAIT: begin
        cache_addr = {addr_rw[31:LINE_WORDS_WIDTH+2], word_count_buf,
2'b00};

        cache_din = mem_data_syn;
        cache_store = mem_ack_syn;

    end

endcase

endcase
```

Output (2)



```
case (next_state)
    S_IDLE, S_BACK_WAIT, S_FILL_WAIT: begin
        mem_cs_o <= 0;
        mem_we_o <= 0;
        mem_addr_o <= 0;
    end
    S_BACK: begin
        mem_cs_o <= 1;
        mem_we_o <= 1;
        mem_addr_o <= {cache_tag, addr_rw[31-
TAG_BITS:LINE_WORDS_WIDTH+2], next_word_count, 2'b00};
    end
    S_FILL: begin
        mem_cs_o <= 1;
        mem_we_o <= 0;
        mem_addr_o <= {addr_rw[31:LINE_WORDS_WIDTH+2],
next_word_count, 2'b00};
    end
endcase
```

Simulation (1)



```
module inst (  
    input wire clk,  
    input wire rst,  
    input wire [3:0] index, // instruction index  
    output wire valid, // stop running if valid is 0  
    output wire write, // write enable signal for cache  
    output wire [31:0] addr // address for cache  
);  
reg [33:0] data [0:7];  
initial begin // clock cycles are only for reference  
    data[0] = 34'h200000004; // read miss      1+17  
    data[1] = 34'h300000018; // write miss    1+17  
    data[2] = 34'h200000008; // read hit      1  
    data[3] = 34'h300000014; // write hit     1  
    data[4] = 34'h210000004; // read & clean replace 1+17  
    data[5] = 34'h310000018; // write & dirty replace 1+17*2  
    data[6] = 34'h310000008; // write hit     1  
    data[7] = 34'h0;        // end          total: 92  
  
end  
assign  
  
    valid = data[index][33],  
    write = data[index][32],  
    addr = data[index][31:0];
```

Simulation (2)



```
`timescale 1ns / 1ps
```

```
module top (  
    input wire clk,  
    input wire rst,  
    output reg [7:0] clk_count = 0,  
    output reg [7:0] inst_count = 0,  
    output reg [7:0] hit_count = 0  
);
```

```
// instruction  
reg [3:0] index = 0;  
wire valid;  
wire write;  
wire [31:0] addr;  
wire stall;  
inst INST (  
    .clk(clk),  
    .rst(rst),  
    .index(index),  
    .valid(valid),  
    .write(write),  
    .addr(addr)
```

```
always @(posedge clk) begin  
    if (rst)  
        index <= 0;  
    else if (valid && ~stall)  
        index <= index + 1'h1;  
end  
// ram  
wire mem_cs;  
wire mem_we;  
wire [31:0] mem_addr;  
wire [31:0] mem_din;  
wire [31:0] mem_dout;  
wire mem_ack;  
data_ram #(  
    .ADDR_WIDTH(5),  
    .CLK_DELAY(3)  
    ) RAM (  
    .clk(clk),  
    .rst(rst),  
    .addr({26'b0, mem_addr[5:0]}),  
    .cs(mem_cs),  
    .we(mem_we),  
    .din(mem_din),  
    .dout(mem_dout),  
    .stall(),  
    .ack(mem_ack)  
);
```

Simulation (3)



```
// cache
cmu CMU (
    .clk(clk),
    .rst(rst),
    .addr_rw(addr),
    .en_r(~write),
    .data_r(),
    .en_w(write),
    .data_w({16'h5678, clk_count, inst_count}),
    .stall(stall),
    .mem_cs_o(mem_cs),
    .mem_we_o(mem_we),
    .mem_addr_o(mem_addr),
    .mem_data_i(mem_dout),
    .mem_data_o(mem_din),
    .mem_ack_i(mem_ack)
);
```

```
// counter
reg stall_prev;

always @(posedge clk) begin
    if (rst)
        stall_prev <= 0;
    else
        stall_prev <= stall;
end

always @(posedge clk) begin
    if (rst) begin
        clk_count <= 0; // 时钟计数
        inst_count <= 0; // 指令计数
        hit_count <= 0; // 命中计数
    end
    else if (valid) begin
        clk_count <= clk_count + 1'h1;
        inst_count <= index + 1'h1;
        if (~stall_prev && ~stall)
            hit_count <= hit_count + 1'h1;
    end
end

endmodule
```

Simulation (4)



```
module sim_top;
```

```
    // Inputs
```

```
    reg clk;
```

```
    reg rst;
```

```
    // Outputs
```

```
    wire [7:0] clk_count;
```

```
    wire [7:0] inst_count;
```

```
    wire [7:0] hit_count;
```

```
    // Instantiate the Unit Under Test (UUT)
```

```
    top uut (
```

```
        .clk(clk),
```

```
        .rst(rst),
```

```
        .clk_count(clk_count),
```

```
        .inst_count(inst_count),
```

```
        .hit_count(hit_count)
```

```
    );
```

```
    initial begin
```

```
        // Initialize Inputs
```

```
        clk = 0;
```

```
        rst = 1;
```

```
        // Wait 100 ns for global reset to finish
```

```
        #95 rst = 0;
```

```
        // Add stimulus here
```

```
    end
```


```
    initial forever #10 clk = ~clk;
```

```
endmodule
```

Result (1)




- Read miss at 0x00000004

 


Result (2)

 - Write miss at 0x00000018
- Read hit at 0x00000008
- Write hit at 0x00000014




Result (3)

- Read & clean replace at 0x10000004

 

Result (4)

 - Write & dirty replace at 0x10000018
- Write hit at 0x10000008





Performance Analysis

- **Miss Penalty**

- When clean, $MP = 17$
- When dirty, $MP = 34$

- **Result**

- $CLK_COUNT = 92$
- $INST_COUNT = 7$
- $HIT_COUNT = 3$



Checkpoints

- **CP1:**
Waveform Simulation of Cache Line.
- **CP2:**
Waveform Simulation of CMU.



Thanks!