

Computer Architecture Experiment

Topic 6. Pipelined CPU supporting Interrupt

浙江大学计算机学院
陈文智

chenwz@zju.edu.cn



实验操作流程

- 阅读实验文档，理解CP0的工作原理和中断相关机制的实现方式
- 以前一次实验为基础，增加协处理器CP0，支持中断指令及中断相关机制
- 对处理器进行仿真，检验处理器的仿真结果是否符合要求。
- 综合工程并下载至开发板，在单步执行的过程中检查调试屏幕的输出，检验处理器的执行过程是否正确。



实验验收标准

- 仿真执行过程中，处理器的行为和内部控制信号均符合要求。
- 下载至开发板后的单步执行过程中，寄存器的变化过程和最终执行结果与测试程序相吻合。



Outline

- **Experiment Purpose**
- **Experiment Task**
- **Basic Principle**
- **Operating Procedures**
- **Precaution**
- **Checkpoints**



Experiment Purpose

- Understand **the principle of CPU Interrupt and its processing procedure.**
- Understand the function **of CP0 coprocessor.**
- Master **the design methods of pipelined CPU supporting interrupt.**
- master methods of **program verification of Pipelined CPU supporting interrupt.**



Experiment Task

- **Design of Pipelined CPU supporting Interrupt.**
 - Design CPO
 - Design CPU Controller
 - Design datapath
- **Verify the Pipelined CPU with program and observe the execution of program**



What jobs does CP0 do?

- CPU configuration
- Cache control
- **Exception/interrupt control**
- Memory management unit control
- Miscellaneous



Exception/interrupt control

- **CP Instructions**
- **Simple interrupt control**
- **Some Mechanisms**
- **Simple CP0 design**
- **Code Example**




CP Interrupt Instructions (1)


- **Register index bits: 5 bits.**
- **MIPS32 uses another 3 bits “SEL” to extend index bits**
- **CP0 Interrupt Instructions**
 - MTC0
 - MFC0
 - ERET

CP Interrupt Instructions (2)

 
- **Format: MFC0 rt, rd, sel**
- **Function: GPR[rt] = CPR[0, rd, sel]**



 
- **Format: MTC0 rt, rd, sel**
- **Function: CPR[0, rd, sel] = GPR[rt]**



- **ERET**

 

Simple interrupt control (1)

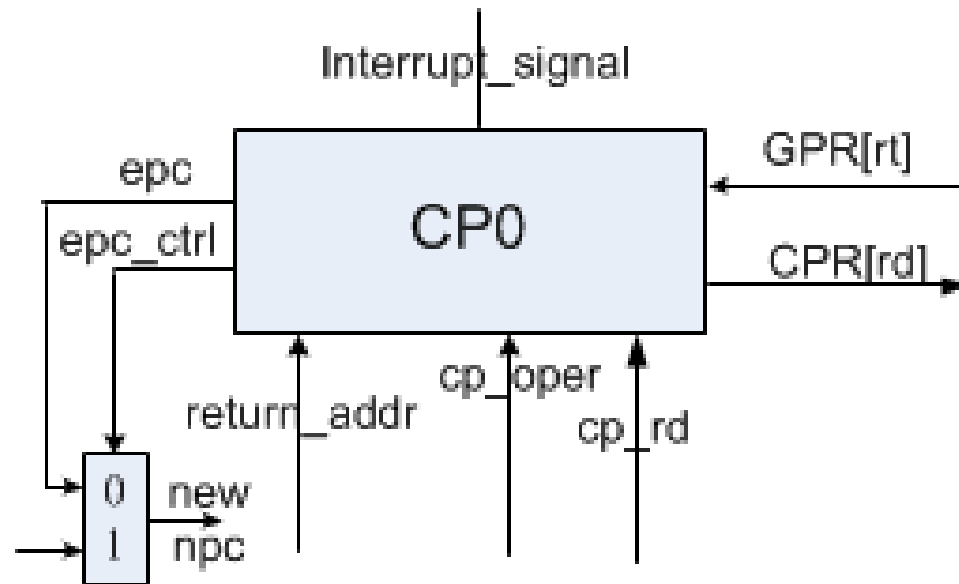

MFC0 rt, rd, sel

#GPR[rt] = CPR[0, rd, sel]

MTC0 rt, rd, sel

#CPR[0, rd, sel] = GPR[rt]



Simple interrupt control (2)

- **Interrupt is detected**
 - Instructions in IF is killed (ID_RST= 1)
 - Return address (Delay slot)
- **Interrupt returns**
 - Modify npc



Some Mechanisms

- **Interrupt signal should be saved**
- **Interrupt handler could not be re-entered**



Simple CP0 design

- **Interrupt register file**
 - Exception Handler Base Register (EHBR)
 - Exception Program Counter Register (EPCR)
- **MTC0: Write Interrupt register file**
- **MFC0: Read Interrupt register file**
- **Interrupt is detected: jump to EHBR (External signal)**
- **ERET: jump to EPCR (From CPU controller)**



Code Example (1)

```
module cp0 (  
    input wire clk, // main clock  
    // debug  
    `ifdef DEBUG  
        input wire [4:0] debug_addr, // debug address  
        output reg [31:0] debug_data, // debug data  
    `endif  
    // operations (read in ID stage and write in EXE stage)  
    input wire [1:0] oper, // CP0 operation type  
    input wire [4:0] addr_r, // read address  
    output reg [31:0] data_r, // read data  
    input wire [4:0] addr_w, // write address  
    input wire [31:0] data_w, // write data  
    // exceptions (check exceptions in MEM stage)  
    input wire rst, // synchronous reset  
    input wire ir_en, // interrupt enable  
    input wire ir_in, // external interrupt input  
    input wire [31:0] ret_addr, // target instruction address to store when interrupt occurred  
    output reg jump_en, // force jump enable signal when interrupt authorised or ERET occurred  
    output reg [31:0] jump_addr // target instruction address to jump to  
);
```



Code Example (2)

```
// interrupt determination
wire ir;
reg ir_wait = 0, ir_valid = 1;
reg eret = 0;
always @(posedge clk) begin
    if (rst)
        ir_wait <= 0;
    else if (ir_in)
        ir_wait <= 1;
    else if (eret)
        ir_wait <= 0;
end
always @(posedge clk) begin
    if (rst)
        ir_valid <= 1;
    else if (eret)
        ir_valid <= 1;
    else if (ir)
        ir_valid <= 0; // prevent exception reenter
end
assign ir = ir_en & ir_wait & ir_valid;
```




Code Example (3)

```
// Exception Handler Base Register  
always @(posedge clk) begin
```

```
.....
```

```
end
```

```
// Exception Program Counter Register  
always @(posedge clk) begin
```

```
.....
```

```
end
```

```
// jump determination  
always @(*) begin
```

```
.....
```


```
end
```



Code Example (4)

- `// CP0 registers`
 - `localparam`
 - `//CP0_SR = 0,`
 - `//CP0_EAR = 1,`
 - `CP0_EPCR = 2,`
 - `CP0_EHBR = 3;`
 - `//CP0_IER = 4,`
 - `//CP0_ICR = 5,`
 - `//CP0_PDBR = 6,`
 - `//CP0_TIR = 7,`
 - `//CP0_WDR = 8;`
- `// EXE CP operations`
 - `localparam`
 - `EXE_CP_NONE = 0,`
 - `EXE_CP_STORE = 1,`
 - `EXE_CP0_ERET = 2;`

Datapath of CPU supporting interrupt.

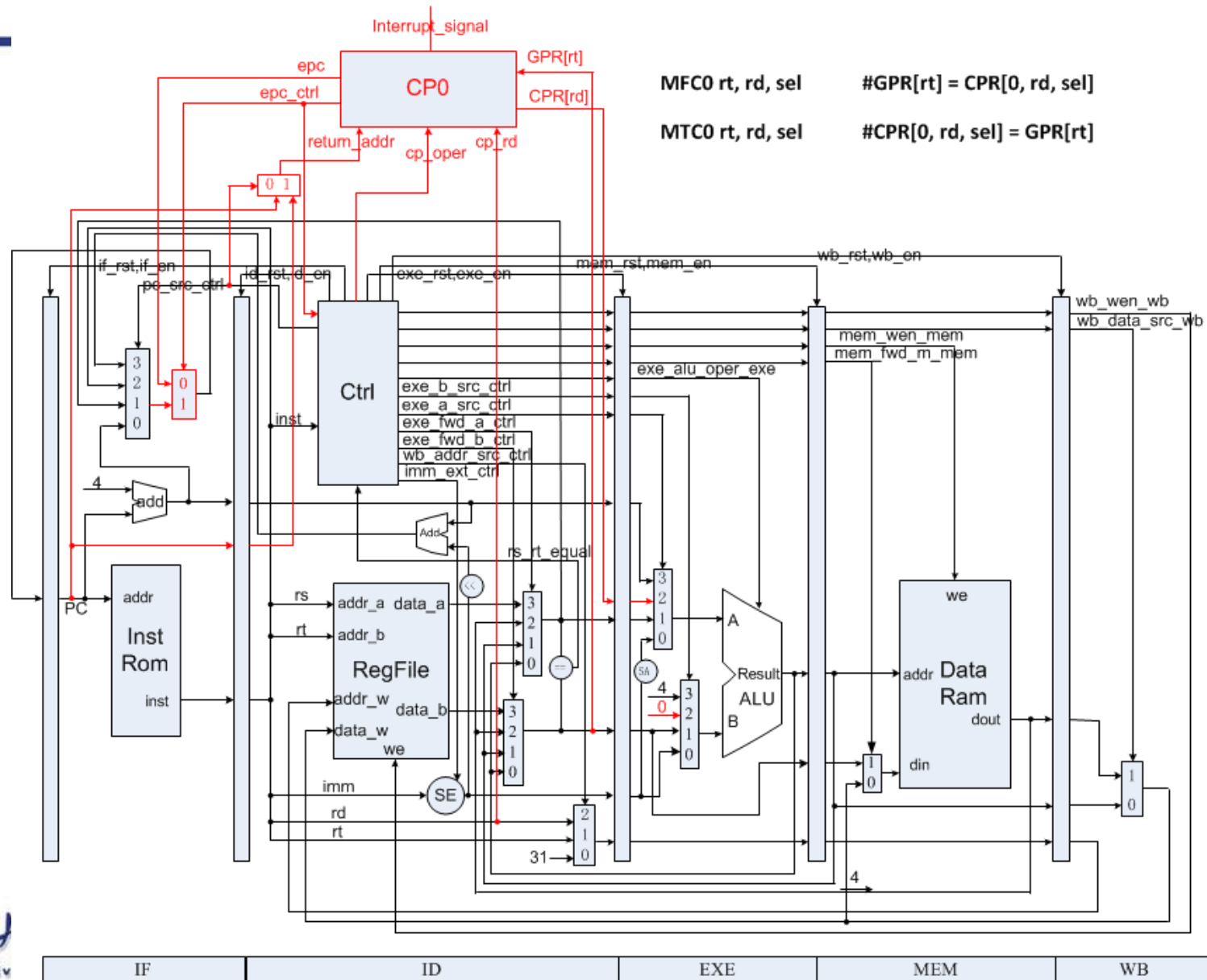



Instr. Mem.(3)

0:	3c010000	lui	R1,0x0	//main entry
4:	24210020	addiu	R1,R1,32	
8:	40811800	mtc0	R1, R3	
c:	00001020	add	R2,R0,R0	
10:	00001820	add	R3,R0,R0	
14:	20420001	addi	R2,R2,1	//loop
18:	08000005	j	14	
1c:	00000000	nop		
20:	40041000	mfc0	R4,R2	//handler
24:	20630001	addi	R3,R3,1	
28:	42000018	eret		
2c:	00000000	nop		











Simulation (4)

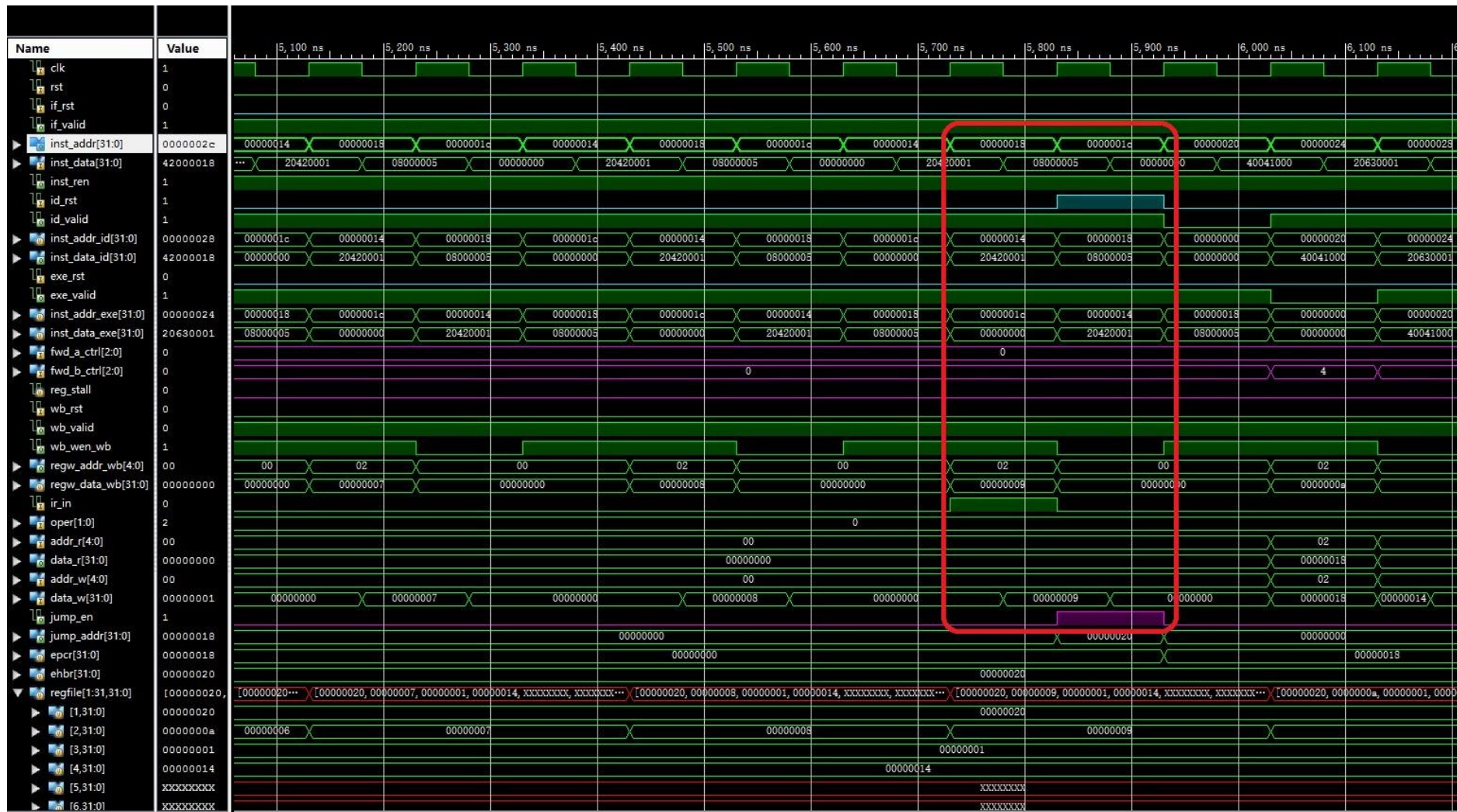

Simulation (5)

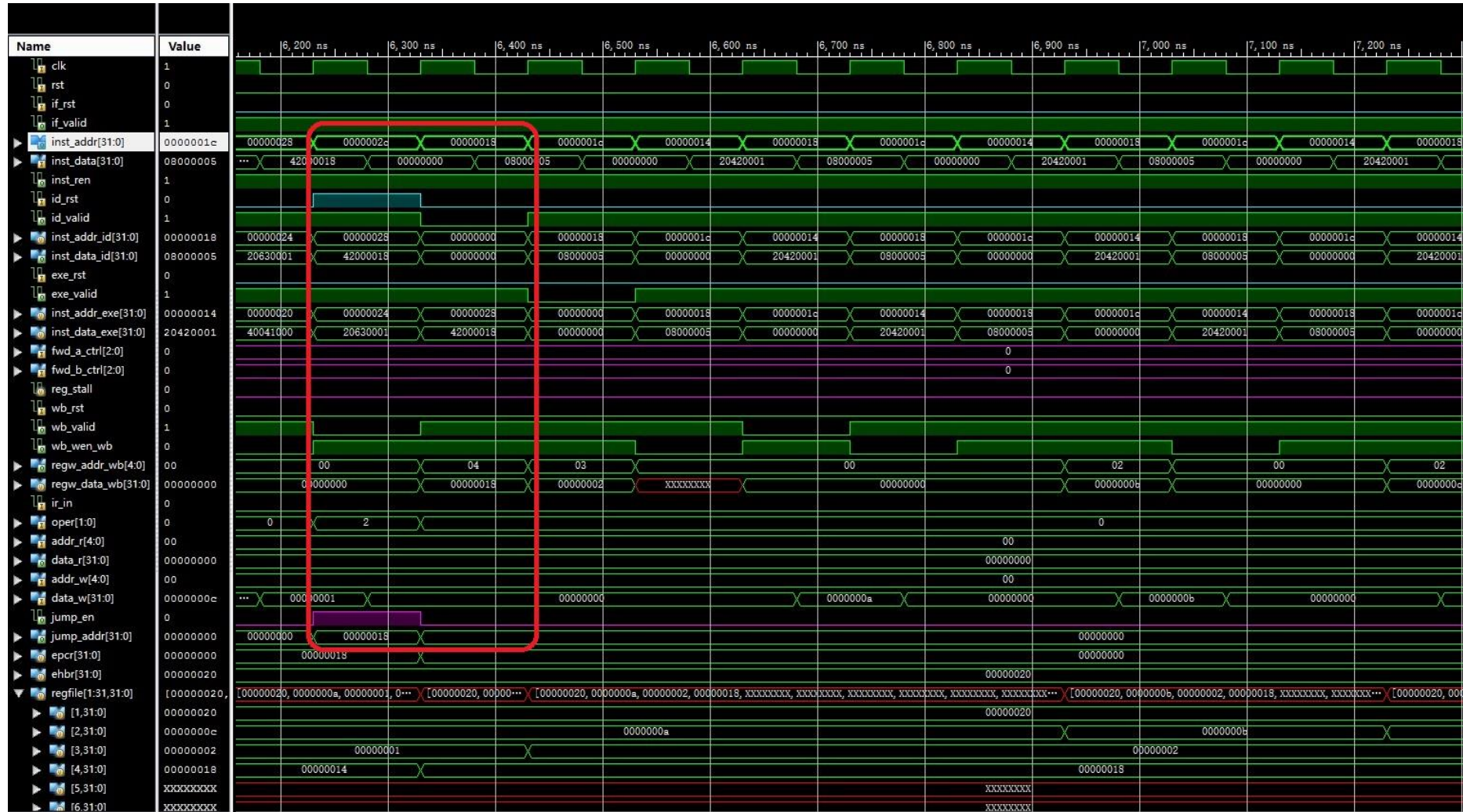



FPGA

- `// interrupt`
 - `wire interrupt;`
 - `reg interrupt_prev;`
 - `always @(posedge clk) begin`
 - `interrupt_prev <= interrupter;`
 - `end`
 - `assign interrupt = ~interrupt_prev & interrupter;`
-
- **Interrupter: West Button**
 - **Interrupt is triggered at posedge of West Button's Pushing**



Checkpoints

- **CP 1:**
Waveform Simulation of the Pipelined CPU
with the verification program
- **CP 2:**
FPGA Implementation of the Pipelined CPU
with the verification program



Thanks!