

# Computer Architecture Experiment

## Topic 2. 5-stage CPU executing in pipeline & Pipelined CPU with stall

浙江大学计算机学院

陈文智

chenwz@zju.edu.cn

---



# 实验操作流程

---

- 阅读实验文档，理解处理器的各个功能模块组成和内部实现方式。
- 补全各个功能模块源代码中的空缺部分。
- 对处理器进行仿真，检验处理器的仿真结果是否符合要求。
- 综合工程并下载至开发板，在单步执行的过程中检查调试屏幕的输出，检验处理器的执行过程是否正确。



# 实验验收标准

---

- 仿真执行过程中，处理器的行为和内部控制信号均符合要求。
- 下载至开发板后的单步执行过程中，寄存器的变化过程和最终执行结果与测试程序相吻合。



# Outline

---

- **Experiment Purpose**
- **Experiment Task**
- **Basic Principle**
- **Operating Procedures**
- **Precaution**
- **Checkpoints**



# Experiment Purpose

---

- Understand **the principles of Pipelined CPU**
- Understand **the basic units of Pipelined CPU**
- Understand **the working flow of 5-stages**
- Understand **the principles of Pipelined CPU Stall**
- Understand **the principles of Data hazard**
- Master **the method of Pipelined CPU Stalls Detection and Stall the Pipeline.**
- Master simulation **of CPU Cores modules**
- master methods of **program verification of Pipelined CPU with Stall**

# Experiment Task




- Design the **CPU Controller**
- Based on the CPU Controller, Design the **Datapath of 5-stages Pipelined CPU**
  - 5 Stages
  - Register File
  - Memory (Instruction and Data)
  - other basic units
- Design the **Stall Part** of Datapath of 5-stages Pipelined CPU
- Adding **Condition Detection** of Stall
- **Simulating CPU Core** module
- **Verify the Pp. CPU with program** and observe the execution of program


# Comparison of three CPUs' work




Simple-Cycle CPU

 


Multiple-Cycle CPU

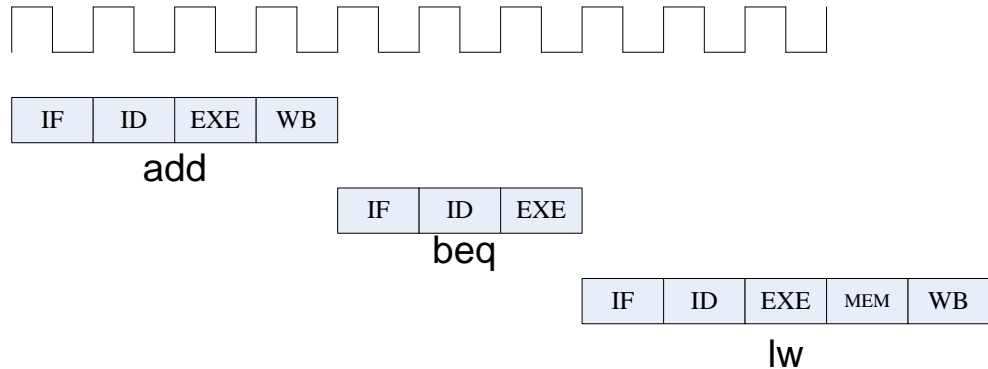

Pipelined CPU

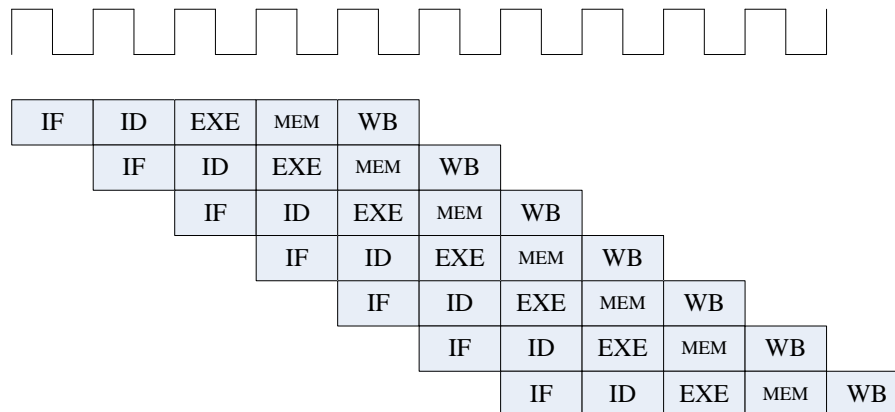


# The principle of Single-cycle CPU

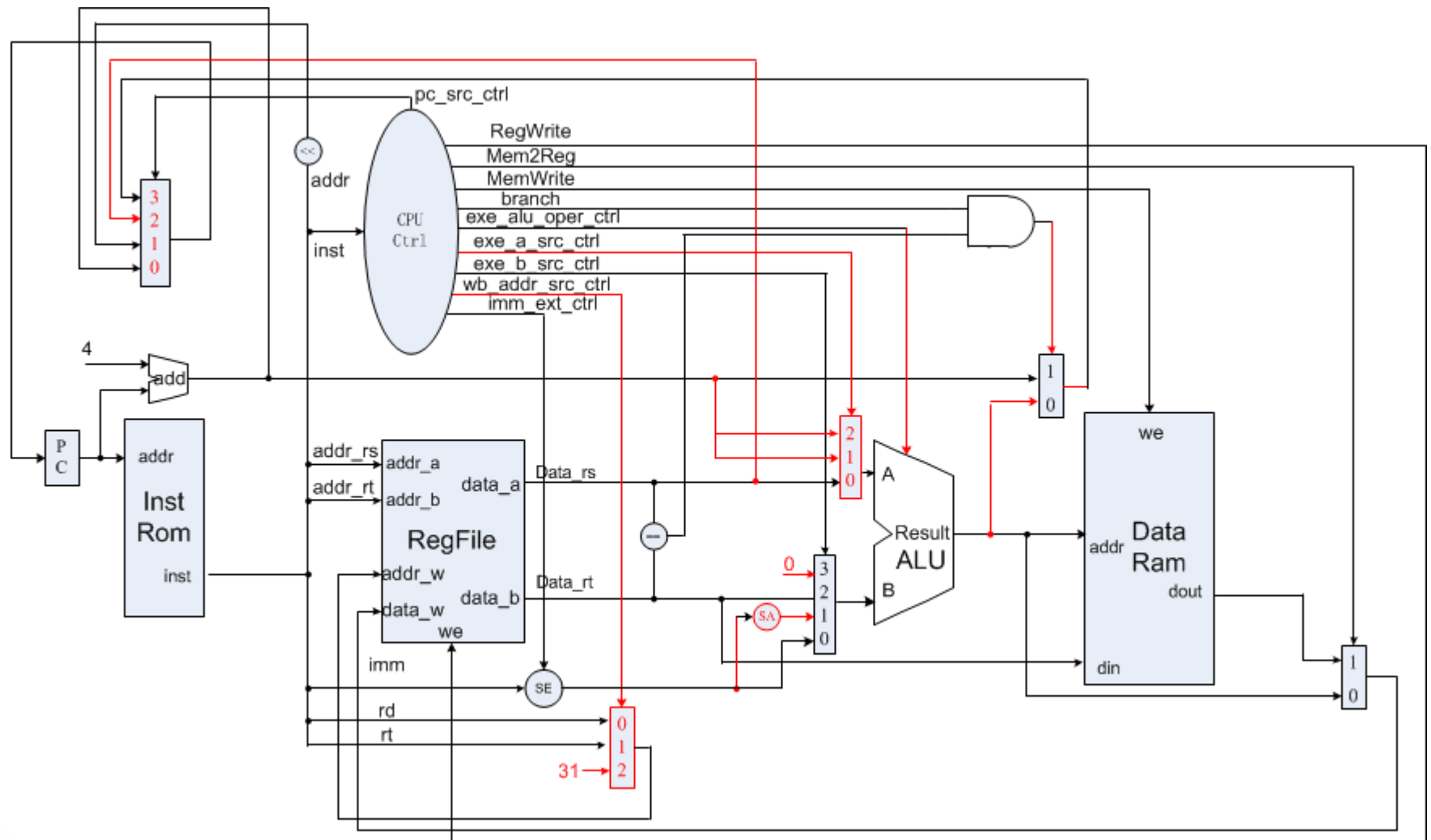



# Datapath of 5-stages Pipelined CPU

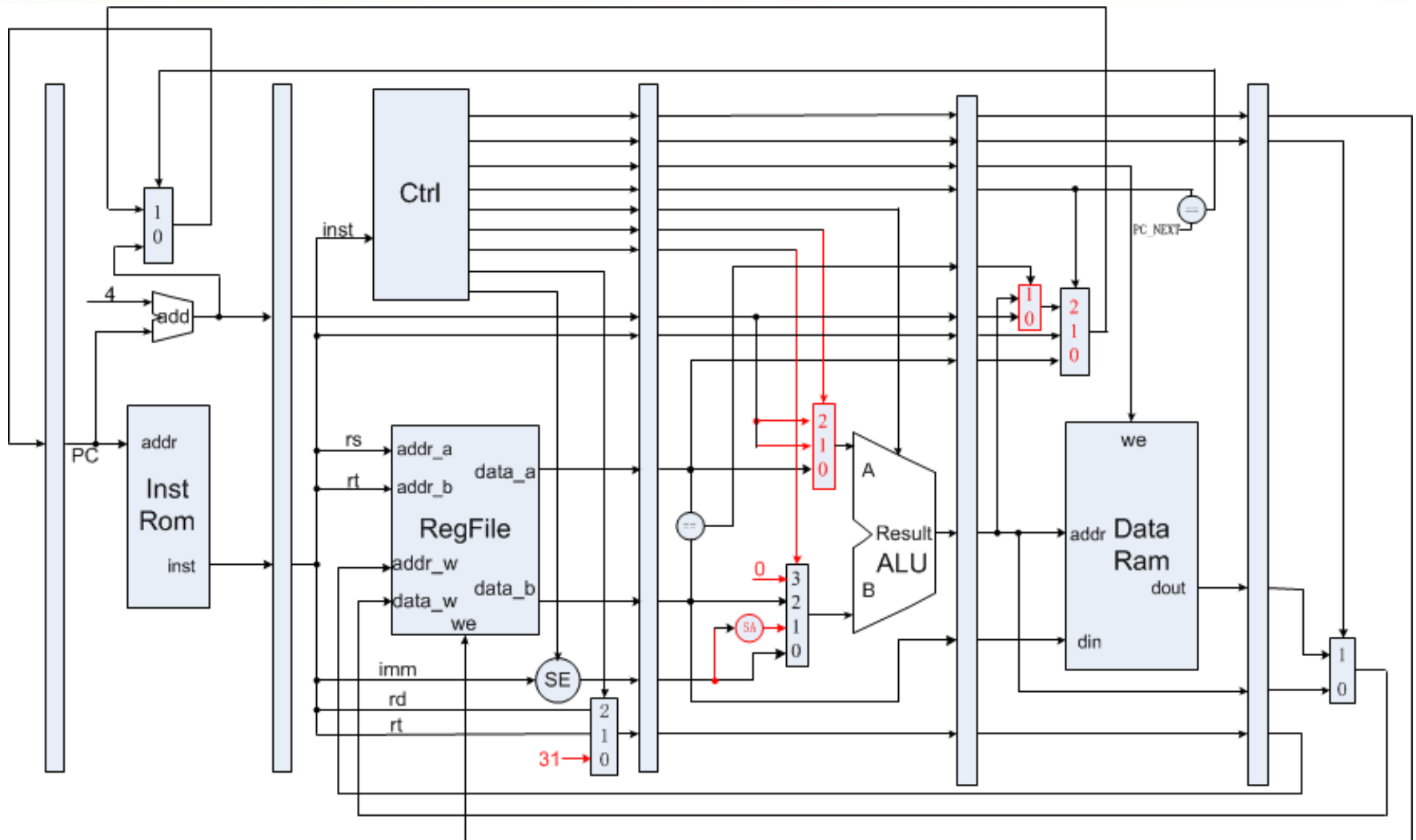


# Structural hazards — resource conflicts



- **Structural hazards arise from resource conflicts when the hardware cannot support all possible combinations of instructions in simultaneous overlapped execution.**
  - Memory conflicts
  - Register File conflicts
  - Other units conflicts

# How to resolve Structural hazards

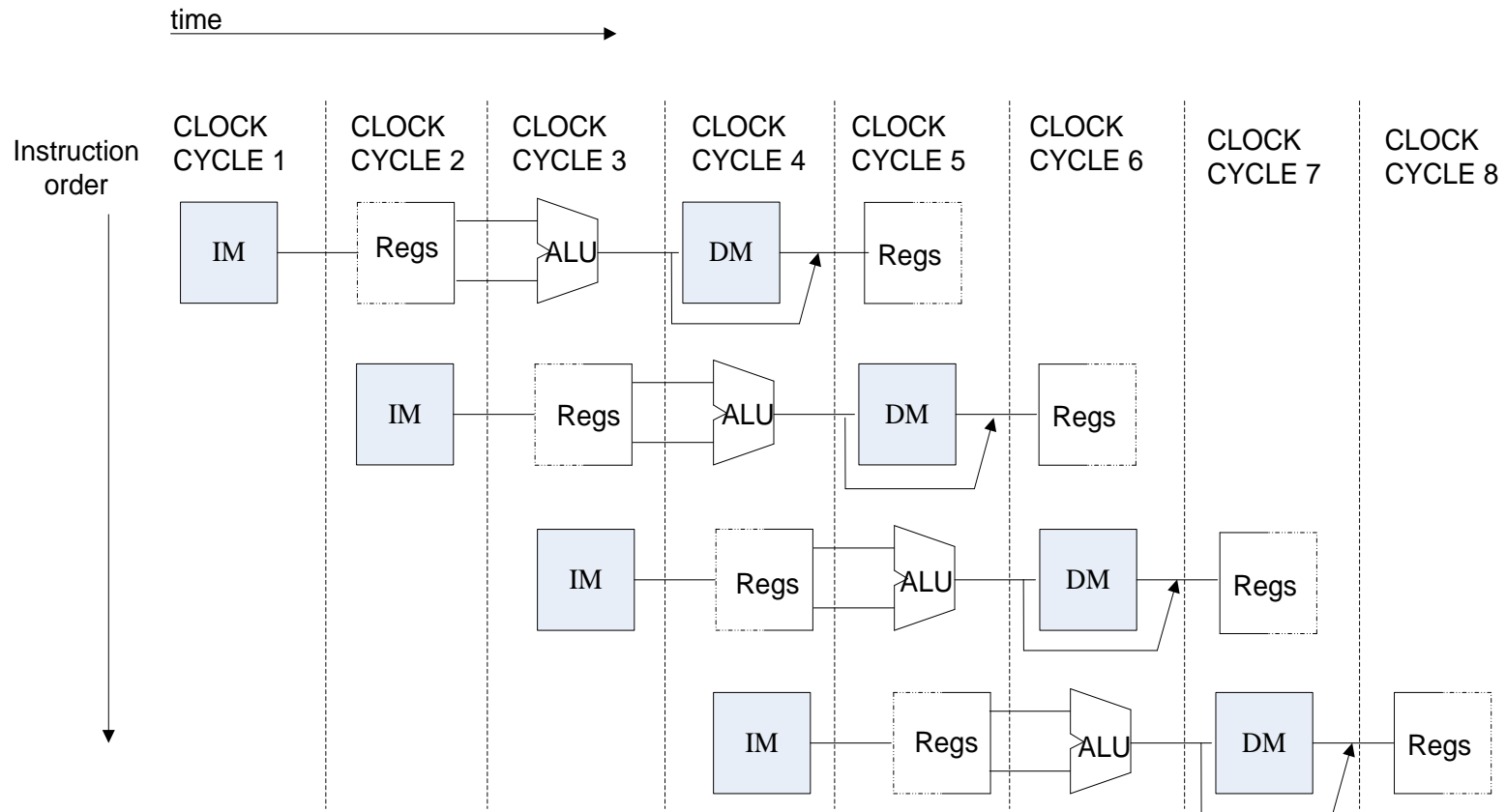



# Memory

---

- **Instruction Memory**
  - Single Port Mem.
  - Read only, Width:32, Depth: 64
  - **Falling** Edge Triggered
- **Data Memory**
  - Single Port Mem.
  - Read and write, Width:32, Depth: 32
  - **Falling** Edge Triggered



# Instruction Memory

```
parameter
    ADDR_WIDTH = 6;
reg [31:0] data [0:(1<<ADDR_WIDTH)-1];
initial begin
    $readmemh("inst_mem.hex", data);
end
reg [31:0] out;
always @(negedge clk) begin
    out <= data[addr[ADDR_WIDTH-1:0]];
end
always @(*) begin
    if (addr[31:ADDR_WIDTH] != 0)
        dout = 32'h0;
    else
        dout = out;
end
```



# Data Memory(1)

---

```
parameter
```

```
    ADDR_WIDTH = 5;
```

```
reg [31:0] data [0:(1<<ADDR_WIDTH)-1];
```

```
initial    begin
```

```
    $readmemh("data_mem.hex", data);
```

```
end
```

```
always @(negedge clk) begin
```

```
    if (we && addr[31:ADDR_WIDTH]==0)
```

```
        data[addr[ADDR_WIDTH-1:0]] <= din;
```

```
end
```



# Data Memory(2)

---

```
reg [31:0] out;
always @(negedge clk) begin
    out <= data[addr[ADDR_WIDTH-1:0]];
end

always @(*) begin
    if (addr[31:ADDR_WIDTH] != 0)
        dout = 32'h0;
    else
        dout = out;
end
```



# Register File

---

- **negative edge for write operation**
- **read operation at any time**
- **Double Bump**





# Register File

```
reg [31:0] regfile [1:31]; // $zero is always zero
// write
always @(negedge clk) begin
    if (en_w && addr_w != 0)
        regfile[addr_w] <= data_w;
end
// read
always @(*) begin
    data_a = addr_a == 0 ? 0 : regfile[addr_a];
    data_b = addr_b == 0 ? 0 : regfile[addr_b];
end
// debug
`ifdef DEBUG
always @(*) begin
    debug_data = debug_addr == 0 ? 0 : regfile[debug_addr];
end
`endif
```



# Timing for Pipelined CPU

---

□ Positive Edge: State Transfer

□ Negative Edge


- Instruction Mem. Read

- Data Mem. Read/Write

- Regfile Write

□ Regfile Read: anytime

# The principle of Pipelined CPU

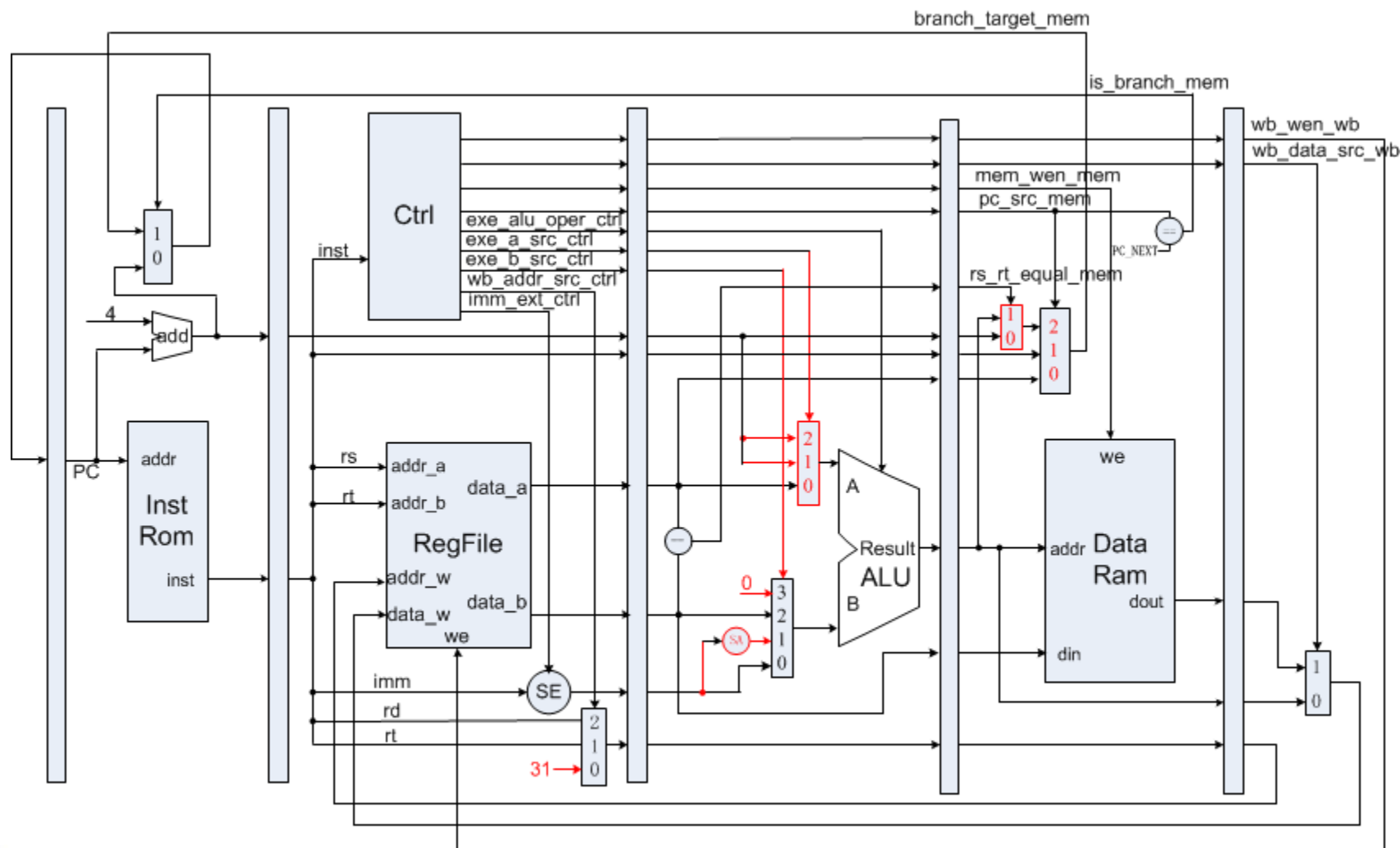


# Data Hazard Definition




- **Data Hazards arise when an instruction depends on the results of a previous instruction in a way that is exposed by the overlapping of instructions in the pipeline.**
- **When inst. i executes before instr. j, there are data hazards:**
  - **RAW**, i.e. instr. j read a source before instr. i writes it.
  - **WAW**, i.e. instr. j write an operand before instr. i writes it.
  - **WAR**, i.e. instr. j write a destination before instr. i read it.

# Instruction Demo

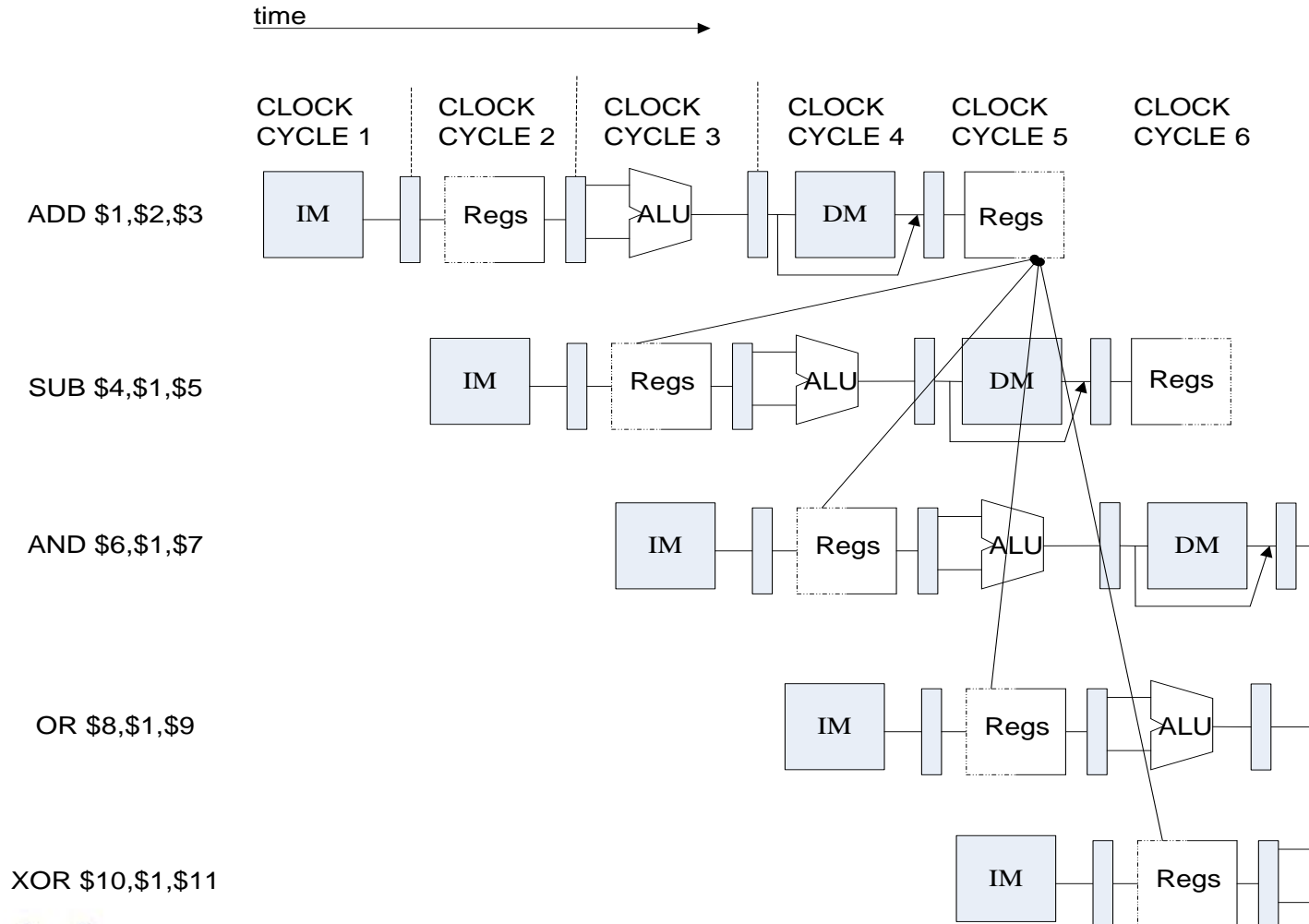

# Data Hazard Causes Stalls

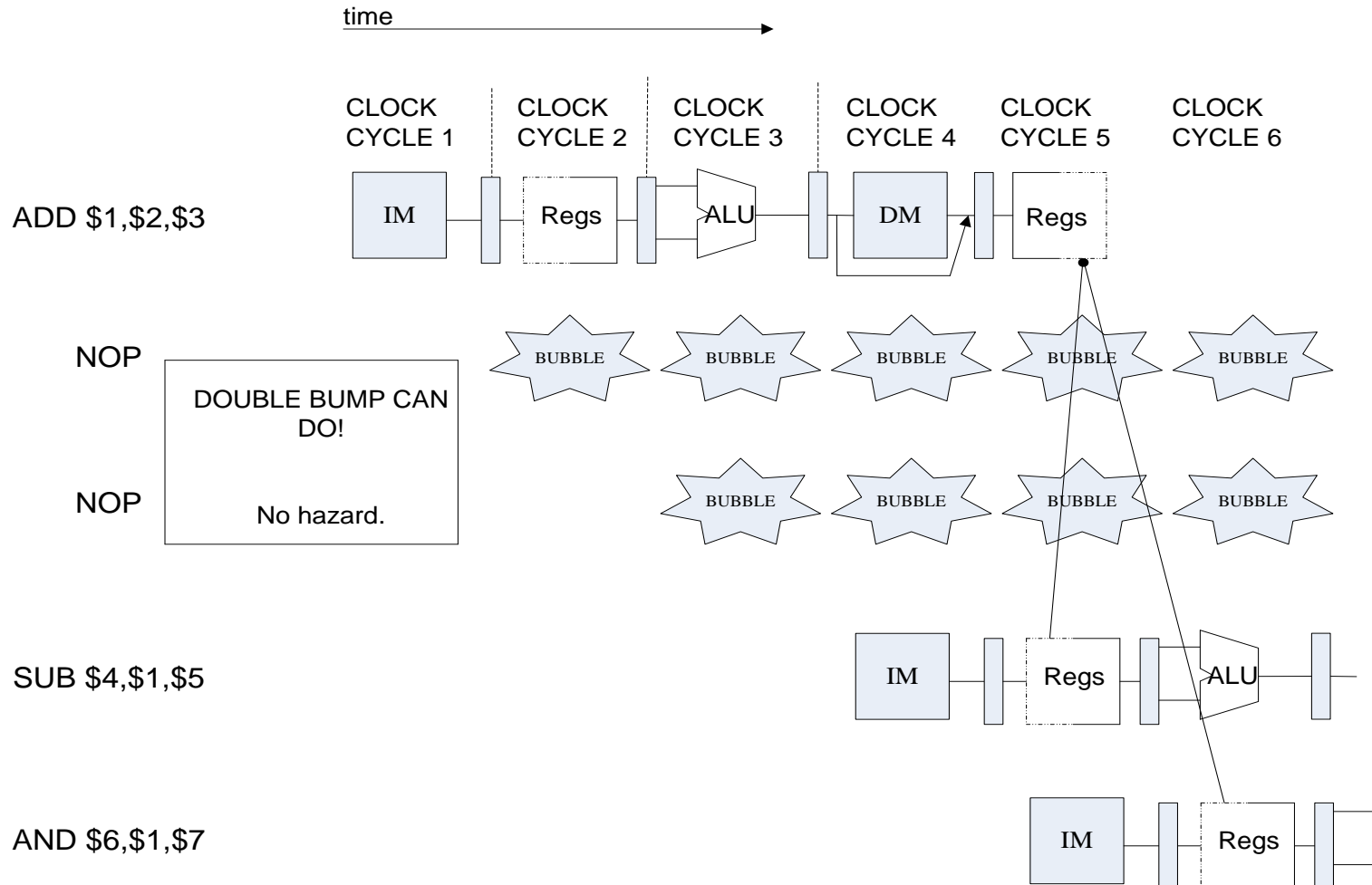




# Control Hazard Definition

---

- **Control Hazards arise from the pipelining of branches and other instructions that change the PC.**




# Execution result

 




# Freeze method

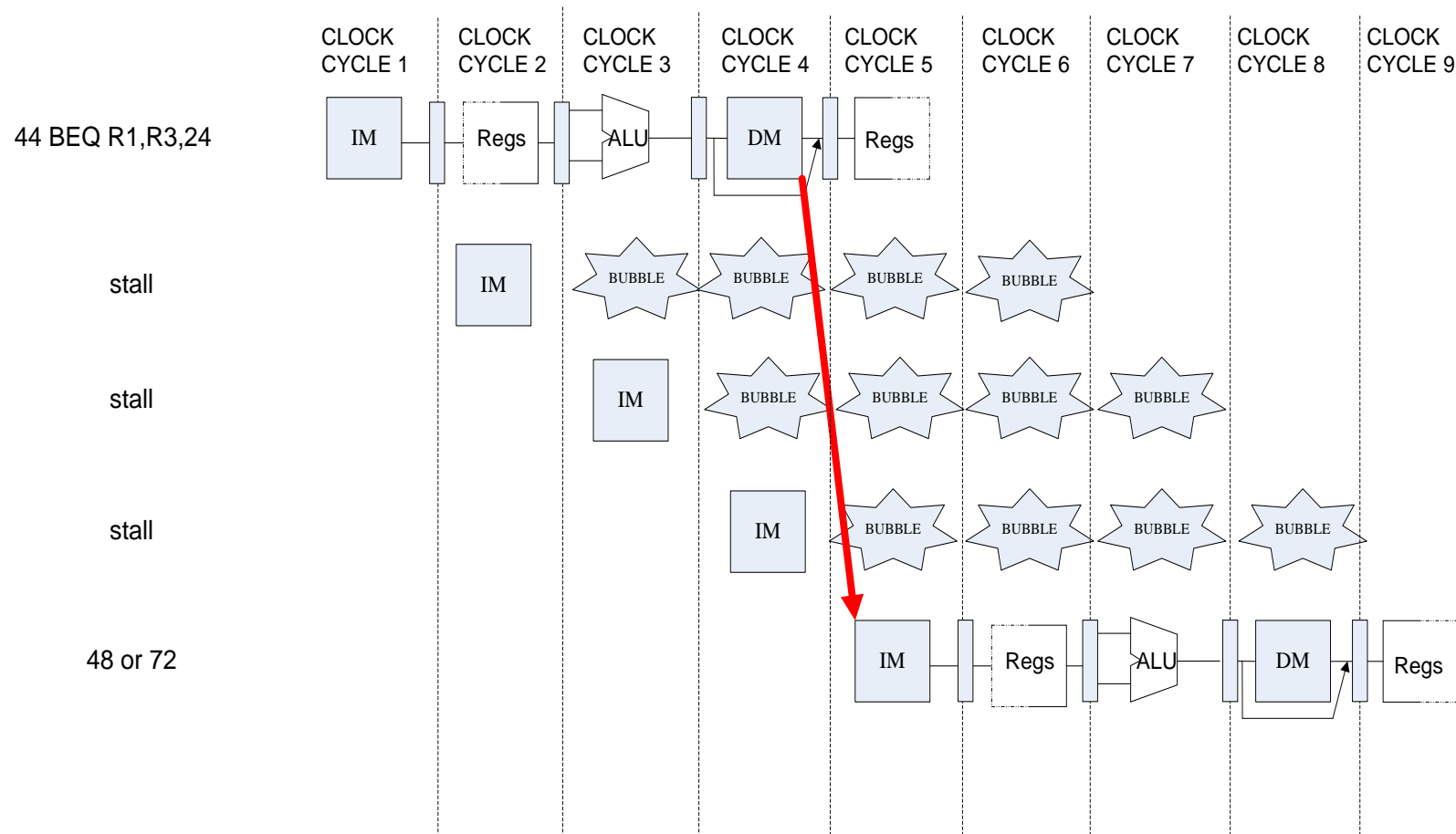

# How to Stall the Pipeline

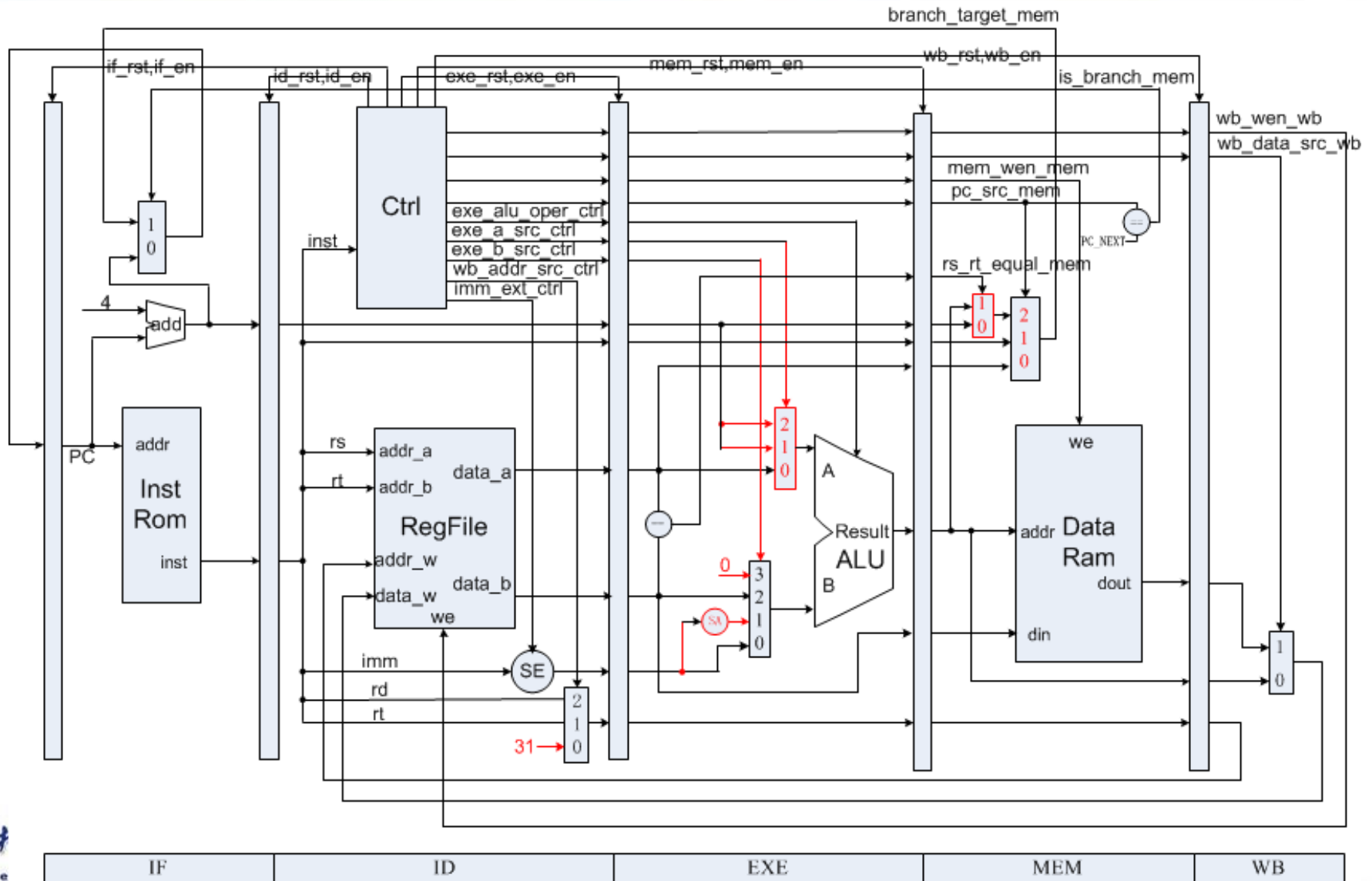



# In Which Conditions it Causes Stall(1)

- **AfromEx** : **//ID instr.rs=exe instr.rd and exe instr.writereg**

```
if (rs_used && addr_rs != 0) begin
    if (regw_addr_exe == addr_rs && wb_wen_exe) begin
        reg_stall = 1;
    end
end
```

- Other expressions:
- **BfromEx**: id instr.rt=ex instr.rd and ex instr.writereg
- **AfromMem**: id instr.rs=mem instr.rd and mem instr.writereg
- **BfromMem** : id instr.rt=mem instr.rd and mem instr = instr.writereg

# In Which Conditions it Causes Stall(2)



- When ID Stage for BEQ INSTR.  
if (pc\_src != PC\_NEXT)  
branch\_stall = 1;
- Other expressions:
- When EXE Stage for BEQ INSTR.
- When MEM Stage for BEQ INSTR.




# Project Introduction

---

- **Top Module**
- **MIPS Core**
- **Instruction Set**
- **Name**
- **Step Execution principle**
- **Observation Info**

# Top Module (1)

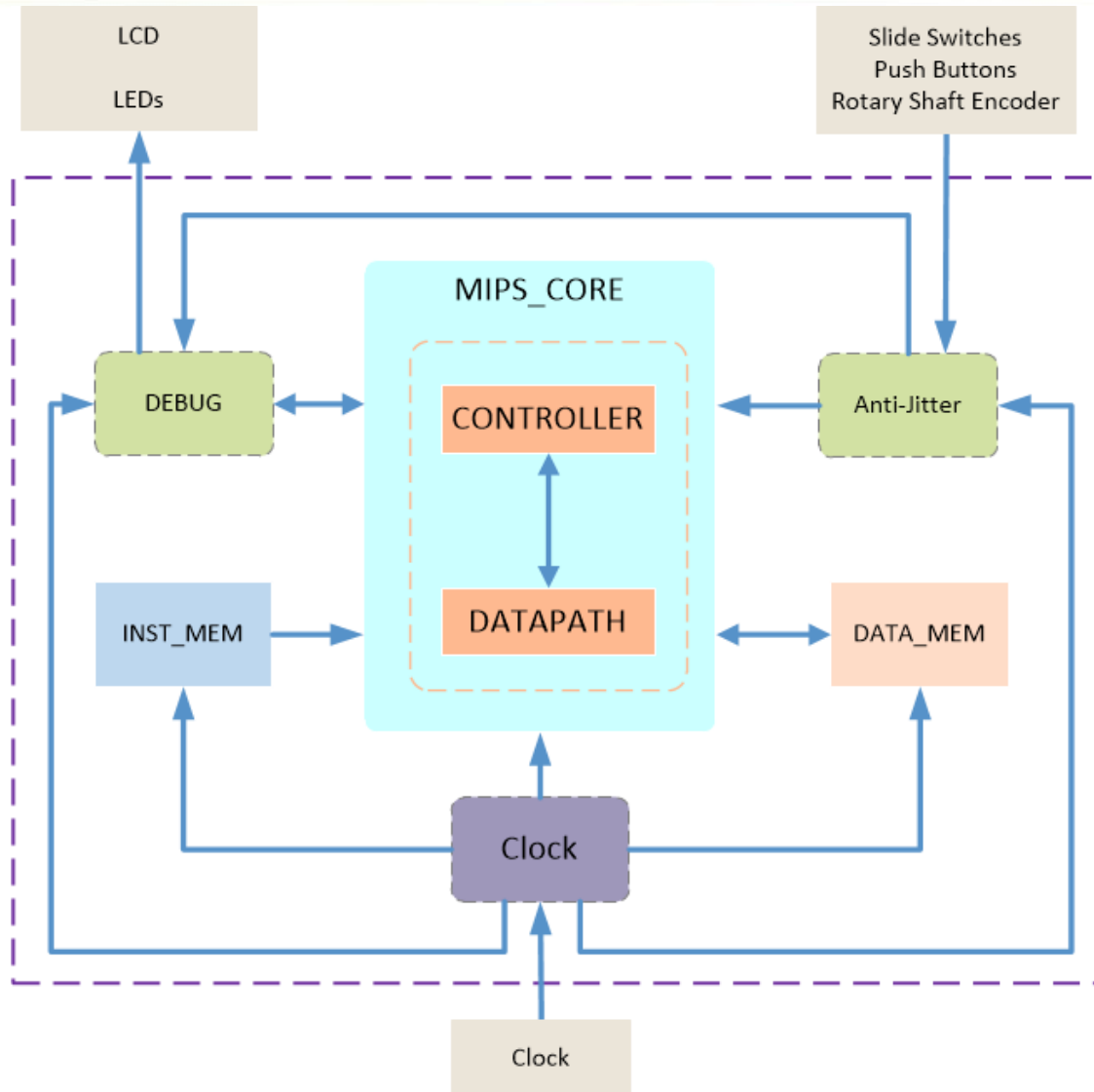



# Top Module (2)

---

- anti-jitter
- clk\_gen
- debug
- mips\_core
- inst\_rom
- data\_ram



# MIPS Core - CPU Controller (1)

---

- CPU Controller works in ID Stage
- Set signals according to different instruction





# MIPS Core - CPU Controller (1)

No.	singals	comment
1	inst	Input for id instruction
2	is_branch_exe	pc src in exe is PC_NEXT or not
3	regw_addr_exe	address source to write data back to registers
4	wb_wen_exe	memory write enable signal
5	is_branch_mem	pc src in mem is PC_NEXT or not
6	regw_addr_mem	address source to write data back to registers
7	wb_wen_mem	memory write enable signal
8	regw_addr_wb	data source of data being written back to registers
9	wb_wen_wb	register write enable signal
10	pc_src	pc src: PC_NEXT, PC_JUMP, PC_JR, PC_BEQ



# MIPS Core - CPU Controller (2)

No.	singals	comment
11	imm_ext	If immediate is extended
12	exe_a_src	Control signal of A operand for ALU
13	exe_b_src	Control signal of B operand for ALU
14	exe_alu_oper	ALU operations
15	mem_ren	Mem read signal
16	mem_wen	Mem write signal
17	wb_addr_src	Control signal of write back addr
18	wb_data_src	Control signal of write back data
19	wb_wen	Control signal of write back enable



# MIPS Core - CPU Controller (3)

No.	singals	comment
21	if_rst/if_en	Output for if stage controll
22	if_valid	Input for if stage stage
23	id_rst/id_en	Output for id stage controll
24	id_valid	Input for id stage stage
25	exe_rst/exe_en	Output for exe stage controll
26	exe_valid	Input for exe stage stage
27	mem_rst/mem_en	Output for mem stage controll
28	mem_valid	Input for mem stage stage
29	wb_rst/wb_en	Output for wb stage controll
30	wb_valid	Input for wb stage stage



# MIPS Core - Datapath

---

- **Debug info output**
- **If subModule**
- **Id subModule**
  - Register file
  - Reg stall logic control
- **Exe subModule**
  - ALU
- **Mem subModule**
- **Wb subModule**

# 16 MIPS Instructions



Bit #	31..26	25..21	20..16	15..11	10..6	5..0	Operations	
R-type	op	rs	rt	rd	sa	func		
add	000000	rs	rt	rd	00000	100000	rd = rs + rt; with overflow	PC+=4
sub		rs	rt	rd	00000	100010	rd = rs - rt; with overflow	PC+=4
and		rs	rt	rd	00000	100100	rd = rs & rt;	PC+=4
or		rs	rt	rd	00000	100101	rd = rs   rt;	PC+=4
sll		00000	rt	rd	sa	000000	rd = rt << sa;	PC+=4
srl		00000	rt	rd	sa	000010	rd = rt >> sa (logical);	PC+=4
slt		rs	rt	rd	00000	101010	if(rs < rt)rd = 1; else rd = 0; <(signed)	PC+=4
jr		rs	00000	00000	00000	001000		PC=rs
I-type	op	rs	rt	immediate				
addi	001000	rs	rt	imm			rt = rs + (sign_extend)imm; with overflow	PC+=4
andi	001100	rs	rt	imm			rt = rs & (zero_extend)imm;	PC+=4
ori	001101	rs	rt	imm			rt = rs   (zero_extend)imm;	PC+=4
lw	100011	rs	rt	imm			rt = memory[rs + (sign_extend)imm];	PC+=4
sw	101011	rs	rt	imm			memory[rs + (sign_extend)imm] <-- rt;	PC+=4
beq	000100	rs	rt	imm			if (rs == rt) PC+=4 + (sign_extend)imm <<2; PC+=4	
J-type	op	address						
j	000010	address					PC = (PC+4)[31..28],address<<2	
jal	000011	address					PC = (PC+4)[31..28],address<<2 ; \$31 = PC+4	



# Name Specification

---

- **Signal of**

- Stage: if, id, exe, mem, wb
- Module: ctrl (id)

- **Signal name**

- xxx\_: works in xxx stage
- \_xxx: generated from xxx stage



# Step Execution Principle

---

- Stall all the stage.
- When step button is pushed, unlock the stall controllers of all the stages.
- Controller:

else if ((debug\_en) && ~(~debug\_step\_prev && debug\_step)) begin

if\_en = 0;

id\_en = 0;

exe\_en = 0;

mem\_en = 0;

wb\_en = 0;

end



# Reg Stall & Branch Stall

**// this stall indicate that ID is waiting for previous instruction, insert one NOP between ID and EXE.**

**else if (reg\_stall) begin**

**if\_en = 0;**

**id\_en = 0;**

**exe\_rst = 1;**

**end**

**//if branch\_stall is on, insert NOP in ID.**

**else if (branch\_stall) begin**

**id\_rst = 1;**

**end**



# Observation Info - Input



- **South Button: Step execution**
- **North Button: Reset**
- **Rotary Shaft Encoder: Index Control**
- **Switich[0]**
  - ❑ 0 for register display
  - ❑ 1 for data signal display: IF-ADDR/ IF-INST/ ID-ADDR/ ID-INST/ EX-ADDR/ EX-INST/ MM-ADDR/ MM-INST/ EMOPER( mem\_ren+ mem\_wen)/ MEMADDR/ MEMDATR/ MEMDATW/.....
- **Switich[3]:**
  - ❑ 0 for run
  - ❑ 1 for step execution

# Observation Info - Output



- LCD
  - ❑ First line: Hello, world (reserved for Cache display)
  - ❑ Second line: Key + value
  
- LED
  - ❑ display for {buttons , switches}'s states



# Program for verification (1)

00000824 main:	and \$1, \$0, \$0	# address of data[0]
34240050	ori \$4, \$1, 80	# address of data[0]
20050004 call:	addi \$5, \$0, 4	# counter
0c00000a	jal sum	# call function
ac820000 return:	sw \$2, 0(\$4)	# store result
8c890000	lw \$9, 0(\$4)	# check sw
ac890004	sw \$9, 4(\$4)	# store result again
01244022	sub \$8, \$9, \$4	# sub: \$8 <- \$9 - \$4
08000008 finish:	j finish	# dead loop
00000000	nop	# done



# Program for verification (2)

00004020	sum:	add \$8, \$0, \$0	# sum function entry
8c890000	loop:	lw \$9, 0(\$4)	# load data
01094020		add \$8, \$8, \$9	# sum
20a5ffff		addi \$5, \$5, -1	# counter - 1
20840004		addi \$4, \$4, 4	# address + 4
0005182a		slt \$3, \$0, \$5	# finish?
1460fffa		bne \$3, \$0, loop	# finish?
01001025		or \$2, \$8, \$0	# move result to \$v0
03e00008		jr \$ra	# return
00000000		nop	# done


# Checkpoints

---




- **CP 1:** Waveform Simulation of 5-stage Pipelined CPU
- **CP 2:** FPGA Implementation of 5-stage Pipelined CPU with the verification program

# Simulation - 1

 




# Simulation - 2

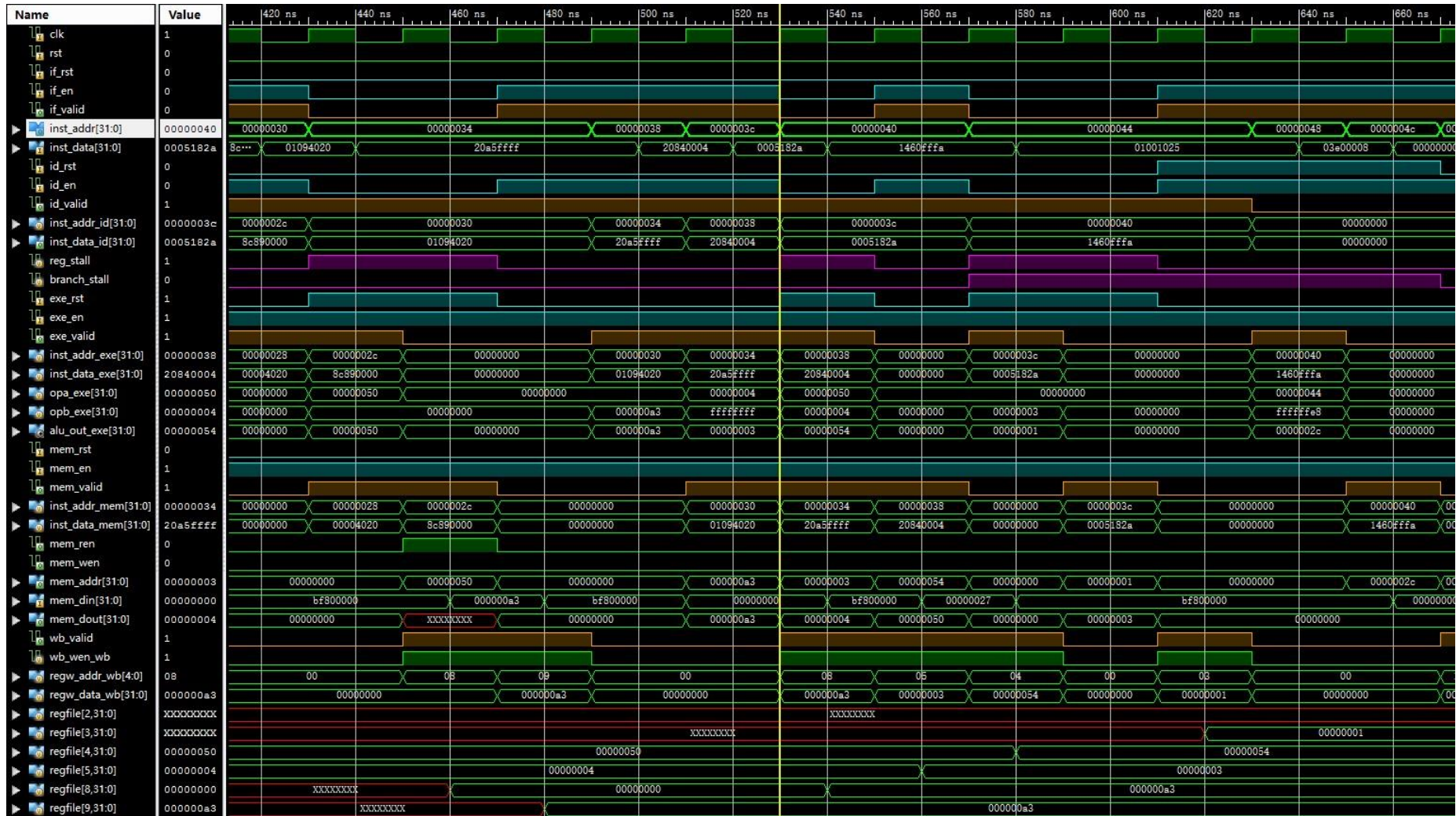

# Simulation - 3

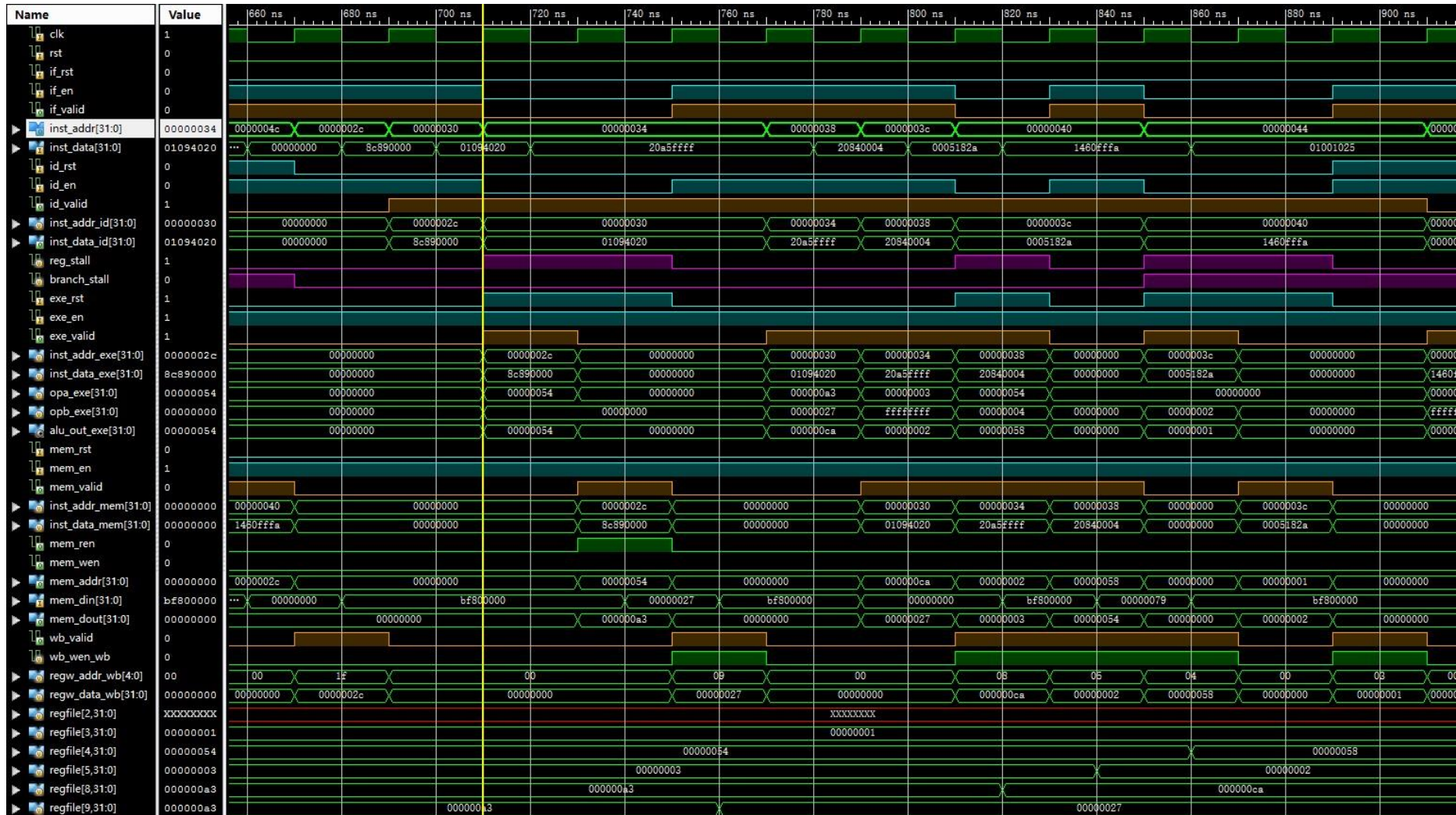



# Settings



Process Properties - Synthesis Options

Switch Name	Property Name	Value
-opt_mode	Optimization Goal	Speed
-opt_level	Optimization Effort	Normal
-iuc	Use Synthesis Constraints File	<input checked="" type="checkbox"/>
-uc	Synthesis Constraints File	...
-keep_hierarchy	Keep Hierarchy	No
-glob_opt	Global Optimization Goal	No
-rtlview	Generate RTL Schematic	Yes
-write_timing_constraints	Write Timing Constraints	Soft
-verilog2001	Verilog 2001	<input checked="" type="checkbox"/>

Property display level: Standard ☒ Display switch names Default

OK Cancel Apply Help



---

# Thanks!